

PRACTICUM DIGITAL SYSTEM

MODUL 7

DIGITAL SYSTEM



By :

Donny Rizal Adhi Pratama


L200183161

INFORMATION TECHNOLOGY

FACULTY OF COMMUNICATION AND INFORMATICS

MUHAMMADIYAH UNIVERSITY OF SURAKARTA

Experiment 1 (NOR Latch)

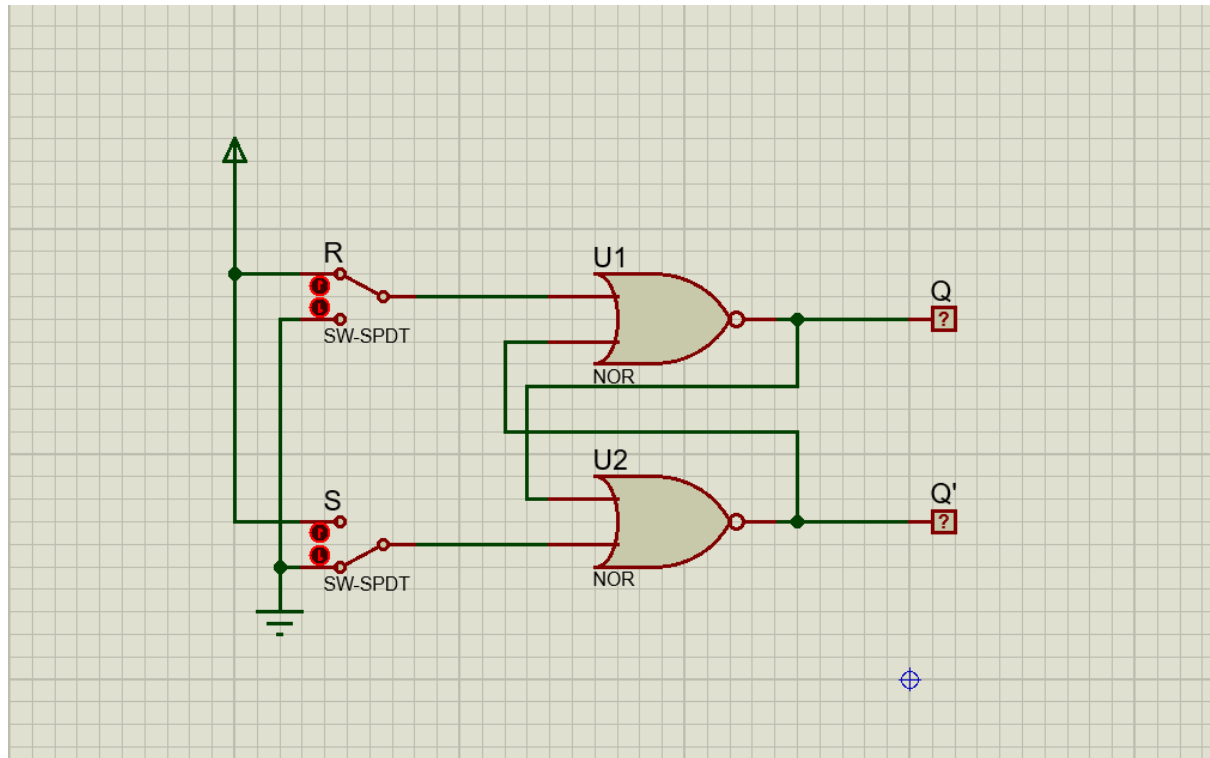


Picture 1.1 NOR Latch

	S (Set)	R (Reset)	Output	
			Q	Q'
1	0	1	0	1
2	0	0	0	1
3	1	0	1	0
4	0	0	1	0
5	1	1	0	0

Answer the question below!

- What will happen if we give the condition $S = R = 0$?
 \Rightarrow The same as before, basically NOR Latch as the storage from output before.
- Why the condition for $S = R = 1$, it is prohibited?
 \Rightarrow Because it can't be the same and it will give the output 0

Experiment 2. (NAND Latch)

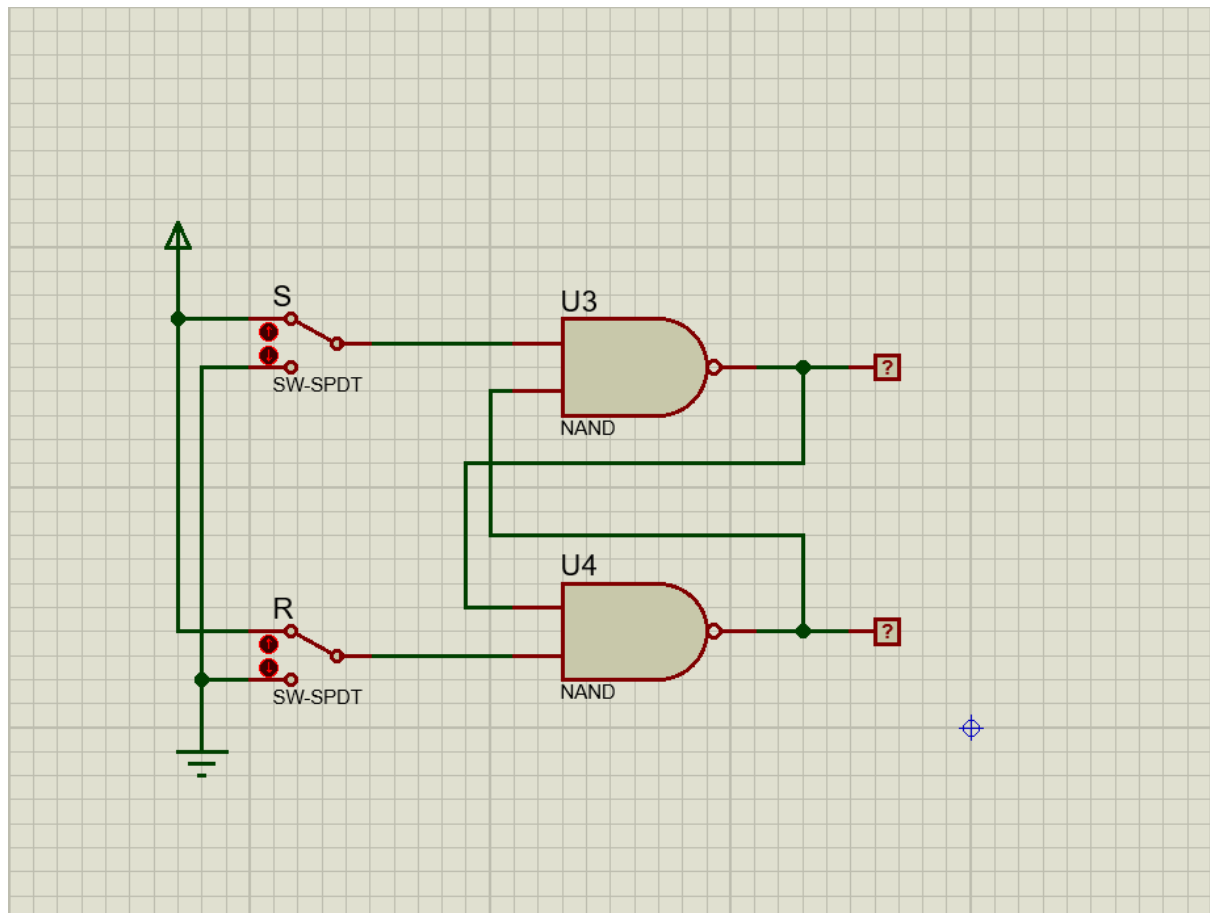

Picture 2.1 NAND Latch

	S (Set)	R (Reset)	Output	
			Q	Q'
1	0	1	1	0
2	1	1	1	0
3	1	0	0	1
4	1	1	0	1
5	0	0	1	1


Answer the question below!

- What will happen if we give the condition for $S = R = 1$?
 \Rightarrow As the data storage before, I mean it will give the output the same as before.
- Why the condition $S = R = 0$ is prohibited?
 \Rightarrow Because it can be the same and will give the output 1

Based on the Circuit flip-flop above, what is your opinion about the statement “Flip-flop and latch use for an Element Storage data”?

- \Rightarrow
- Yes, it is true. Latch as the storage data that use in Electronics that has two stable states to store state Information.

Experiment 3 (Flip Flop RS)

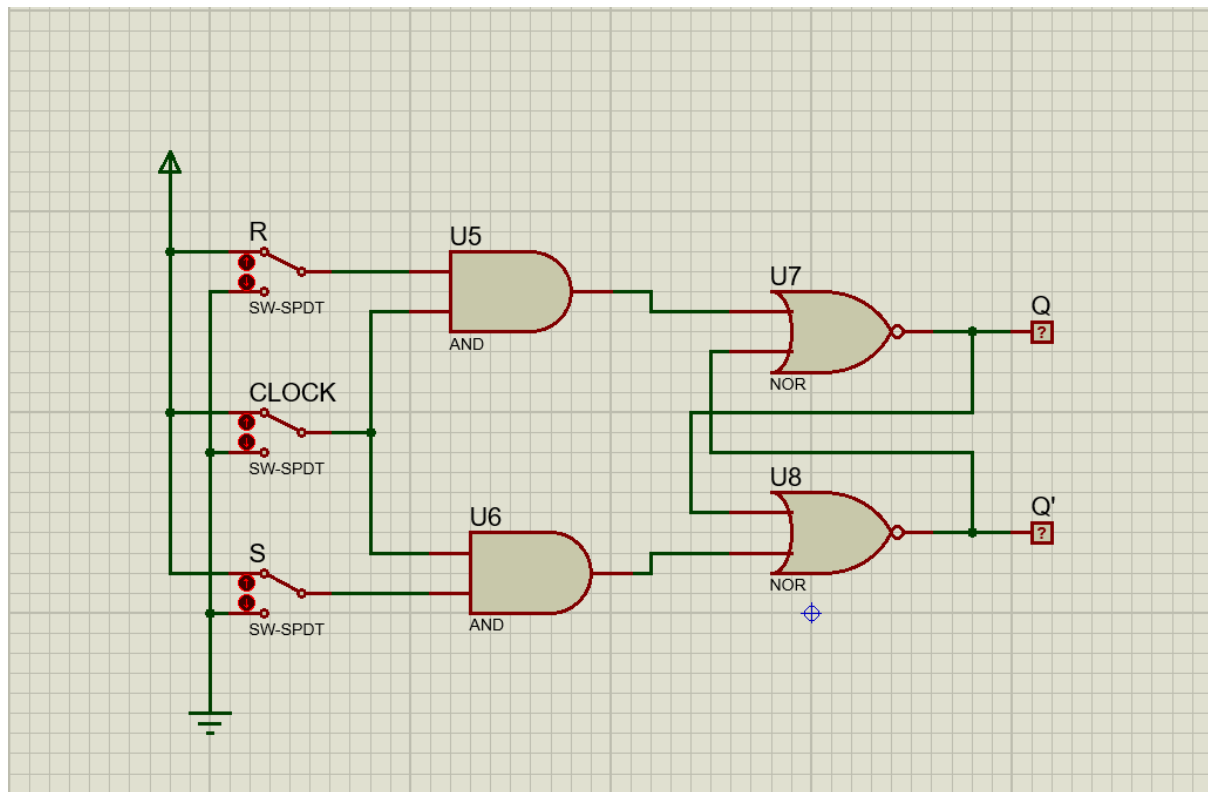

Picture 3.1 Flip – Flop RS

	S (Set)	R (Reset)	Clock	Output	
				Q	$Q_{(t+1)}$
1	0	0	0	--	--
2	0	0	1	--	--
3	0	1	0	--	--
4	0	1	1	0	1
5	1	0	0	0	1
6	1	0	1	1	0
7	1	1	0	1	0
8	1	1	1	0	0

Answer the question below!

- What will happen if we give the condition $S = R = 1$ and the clock changes from 1 into 0?
 \Rightarrow Simulation Error. “Logic race condition detected during transient system”

How that’s possible?

- $$\Rightarrow \text{Because } S = R = 1 \text{ and clock changes from 1 into 0. And it is prohibited the clock in 0 condition.}$$

Explain how Flip – Flop RS Works?


- $$\Rightarrow \text{RS} = 00 \text{ So it will lock the output before}$$
- $$\text{RS} = 01 \text{ it will changes the output } Q \text{ to } Q_{(t+1)}$$

RS = 10 it changes the output Q became 0

RS = 11 the prohibited one and error will occurs.

For the most Clock Has to Not 0 first, When you need to know the result in Flip-Flop RS without error your Clock has to 1 First then change the Set and Reset.

Experiment 4 (Flip – Flop D)

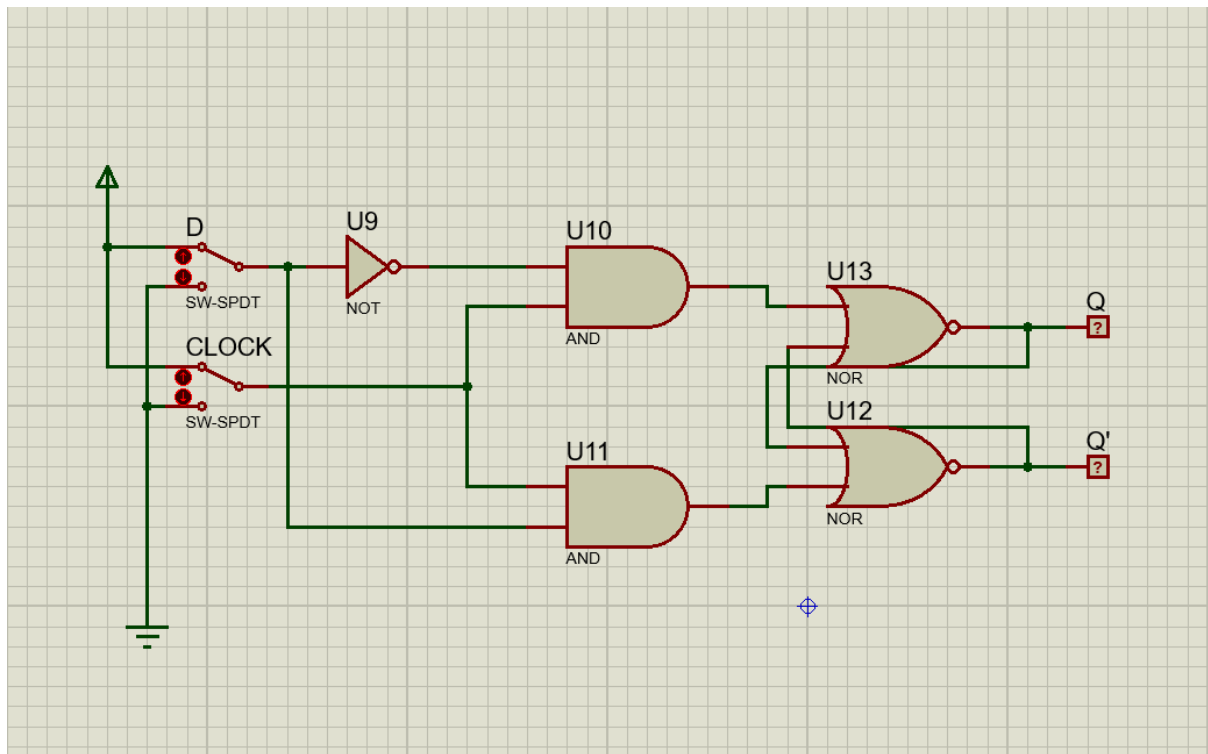

Picture 4.1 Flip Flop D

	D	Clock	Output	
			Q	$Q_{(t+1)}$
1	0	0	--	--
2	0	1	0	1
3	1	0	0	1
4	1	1	1	0
5	0	0	1	0
6	0	1	0	1
7	1	0	0	1
8	1	1	1	0


Explain How Flip – Flop D work!

- ⇒ If Clock Output is 0 so it could be as Latch and lock the Output before
- If Clock Output is 1 so it could change the Output Q

What is the Function of NOT gate in Flip – Flop D compared with Flip – Flop RS!

- ⇒ To solve the Prohibited condition in Flip – Flop RS

Experiment 5 (Flip – Flop JK)

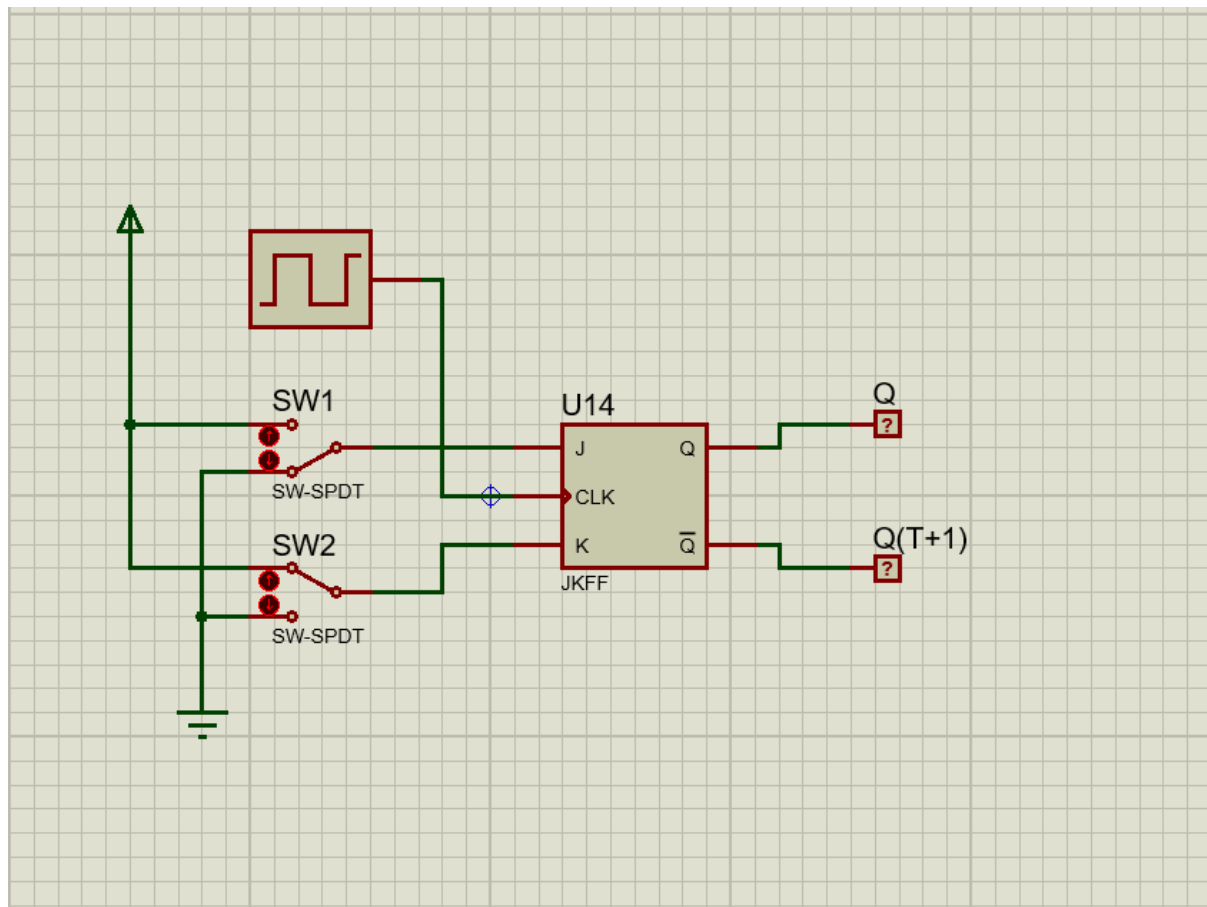

Picture 5.1 Flip – Flop JK

	J	K	Clock	Output	
				Q	$Q_{(t+1)}$
1	0	0	0	0	1
2	0	0	1	0	1
3	0	1	0	0	1
4	0	1	1	0	1
5	1	0	0	1	0
6	1	0	1	1	0
7	1	1	0	1	0
8	1	1	1	1	1

What will happen if $J = K = 0$ and Clock rise up (Change from 0 to 1)?

⇒ Clock output will change overtime but doesn't change the output Q and $Q_{(t+1)}$

What will happen if $J = K = 1$, and Clock Rise Up?

⇒ If the Clock 1 so Output Q and $Q_{(t+1)}$ will be changed too.

⇒ If the Clock 0 so it will store the Output Q and $Q_{(t+1)}$

Explain how Flip – Flop Works!

⇒ How it works it is same as Flip – Flop RS just the prohibited condition ($J = K = 1$, Clock Up) can be done (Solved) .