

PRACTICUM SISDIG

MODUL 4

DIGITAL SYSTEM



By :

Donny Rizal Adhi Pratama


L200183161

INFORMATION TECHNOLOGY

FACULTY OF COMMUNICATION AND INFORMATICS

MUHAMMADIYAH UNIVERSITY OF SURAKARTA

Experiment 1

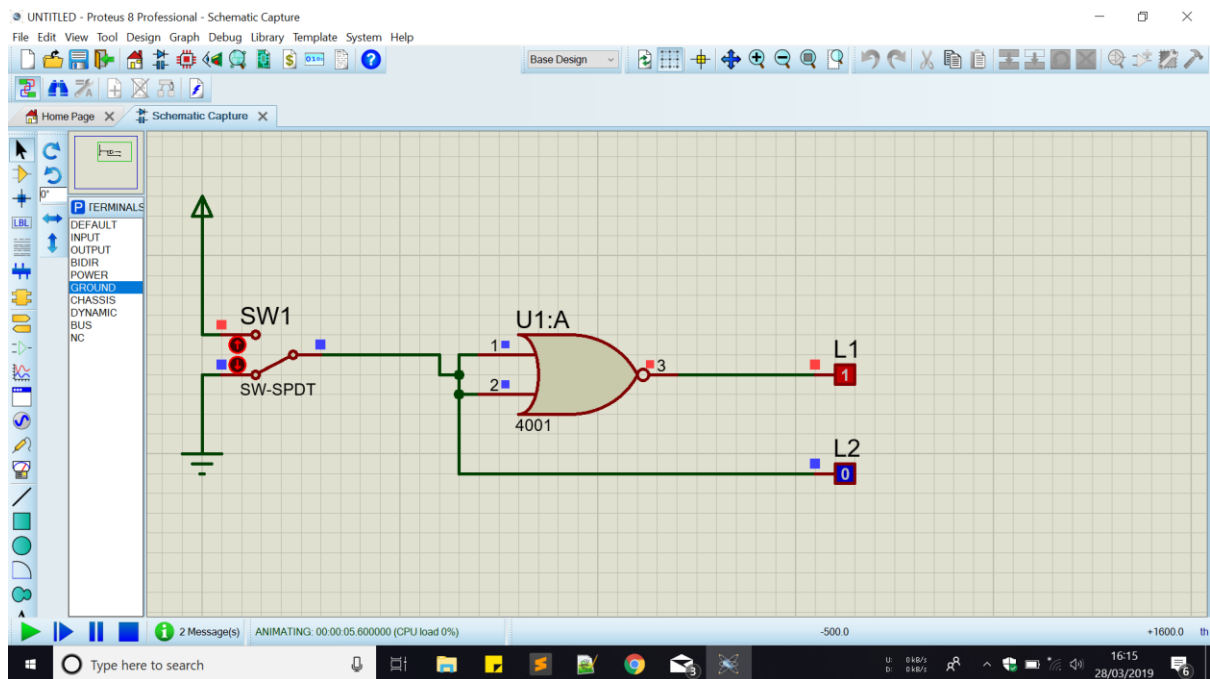

Picture 1.1 Gate 1 Variation

2. Boolean Function : $L1 = \overline{L2} + L2 = \overline{L2}$

3. Truth Table :

SW1	L2	L1
0	0	1
1	1	0


4. Time Diagram

		L1
		L2

5. Conclusion

NOR Gate in the picture above create a logic gate from NOT

Experiment 2.

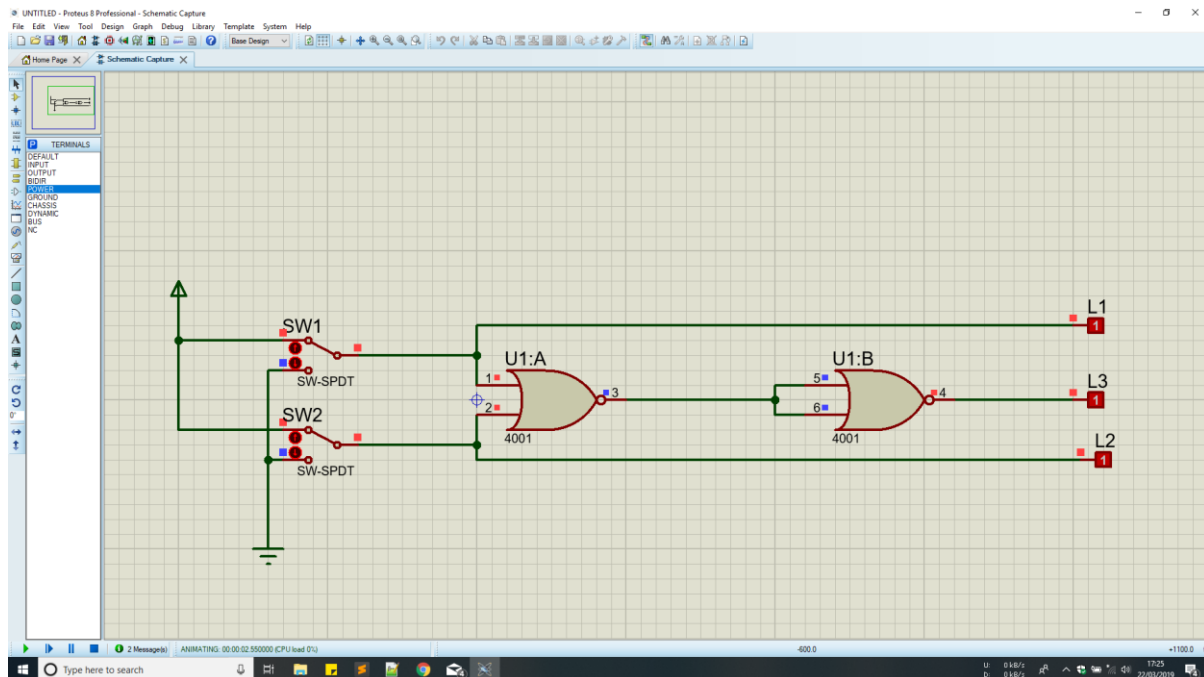

Picture 2.1 Gate 2 Variation

2. Boolean Function : $L3 = \overline{L1 + L2} = L1 + L2$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	1


4. Time Diagram

L1				
L2				
L3				

5. Conclusion

NOR Gate in the picture above create a logic from Gate Or

Experiment 3

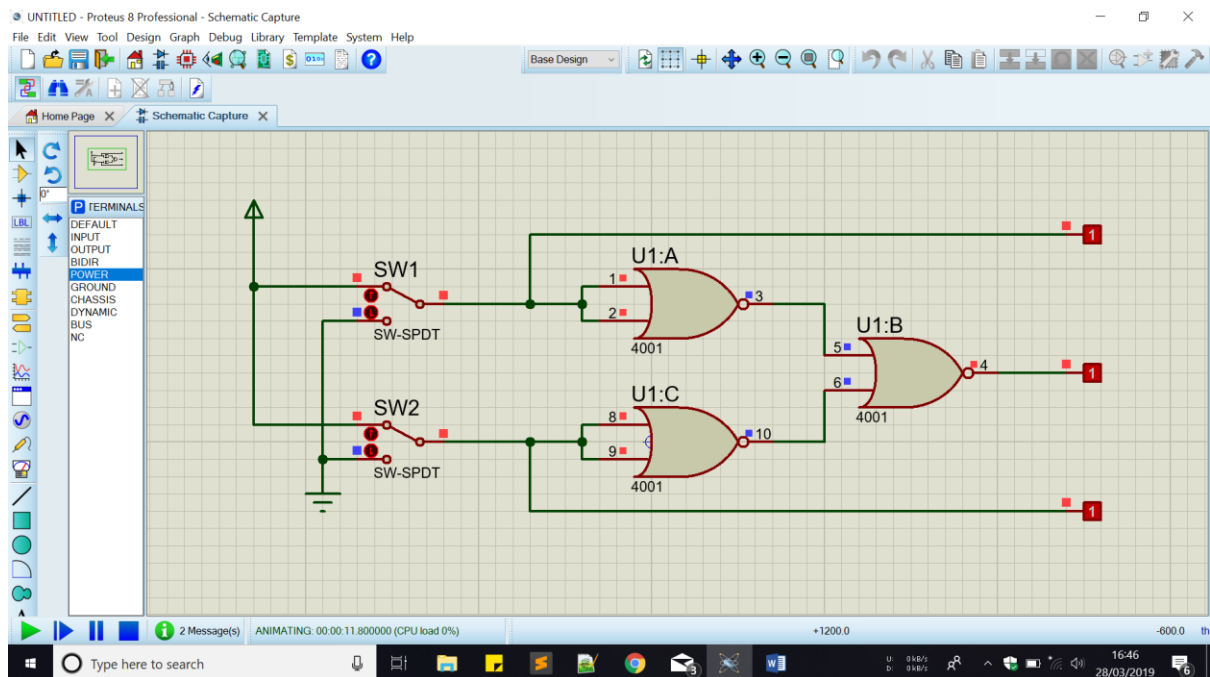

2. Boolean Function : $L3 = \overline{L1} + \overline{L2} = L1 + L2$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
0	1	0	1	0
1	0	1	0	0
1	1	1	1	1


4. Time Diagram

				L1
				L2
				L3

5. Conclusion

Gate NOR in the picture above create logic from Gate AND

Experiment 4

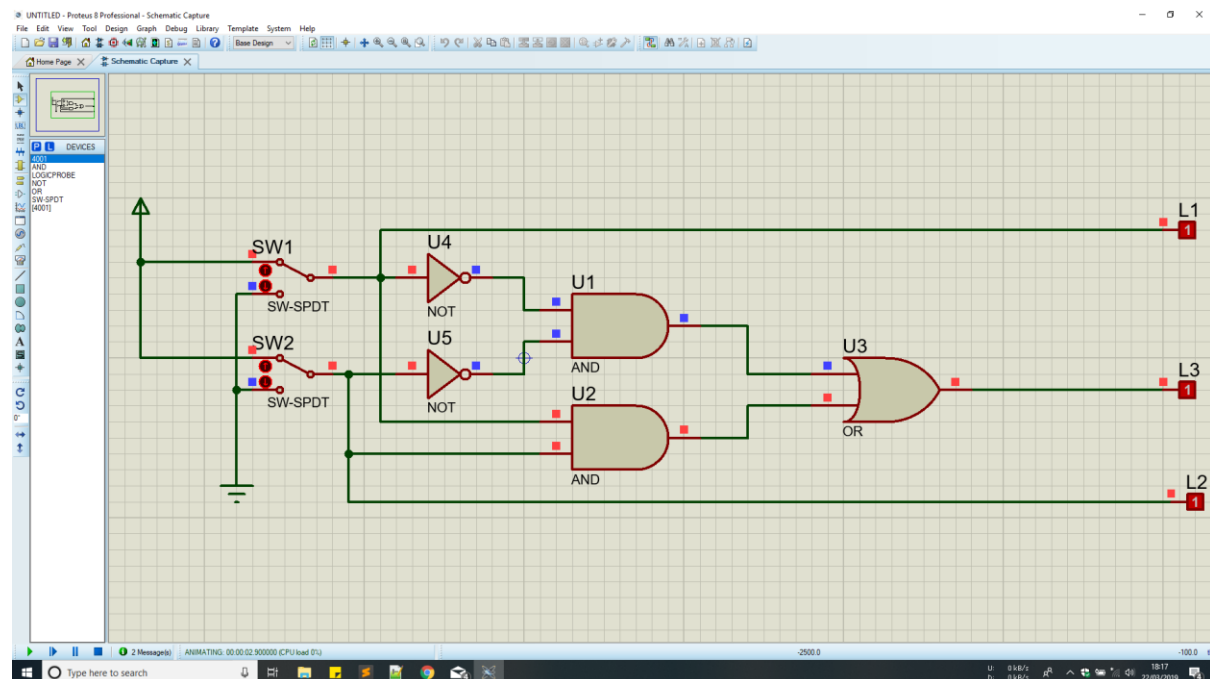

2. Boolean Function : $L3 = \overline{L1} L2 + L1 L2 = \overline{L1} \oplus L2$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	1	1	1


4. Time Diagram

				L1
				L2
				L3

5. Conclusion

Combination Gate in the picture above create logic from Gate XNOR

Experiment 5

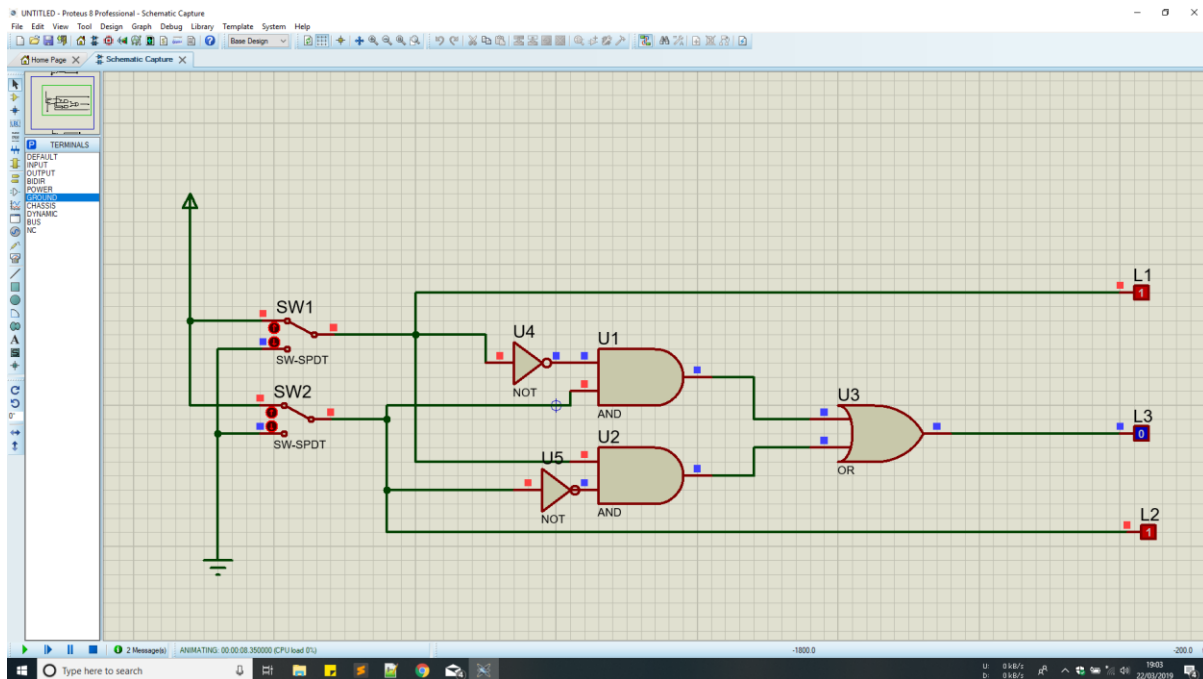

2. Boolean Function : $L3 = \overline{L1}L2 + L1\overline{L2}$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	1	1	0


4. Time Diagram

				L1
				L2
				L3

5. Conclusion

Combinatio Gate in the picture above create logic from Gate XOR

Additional Assignment :

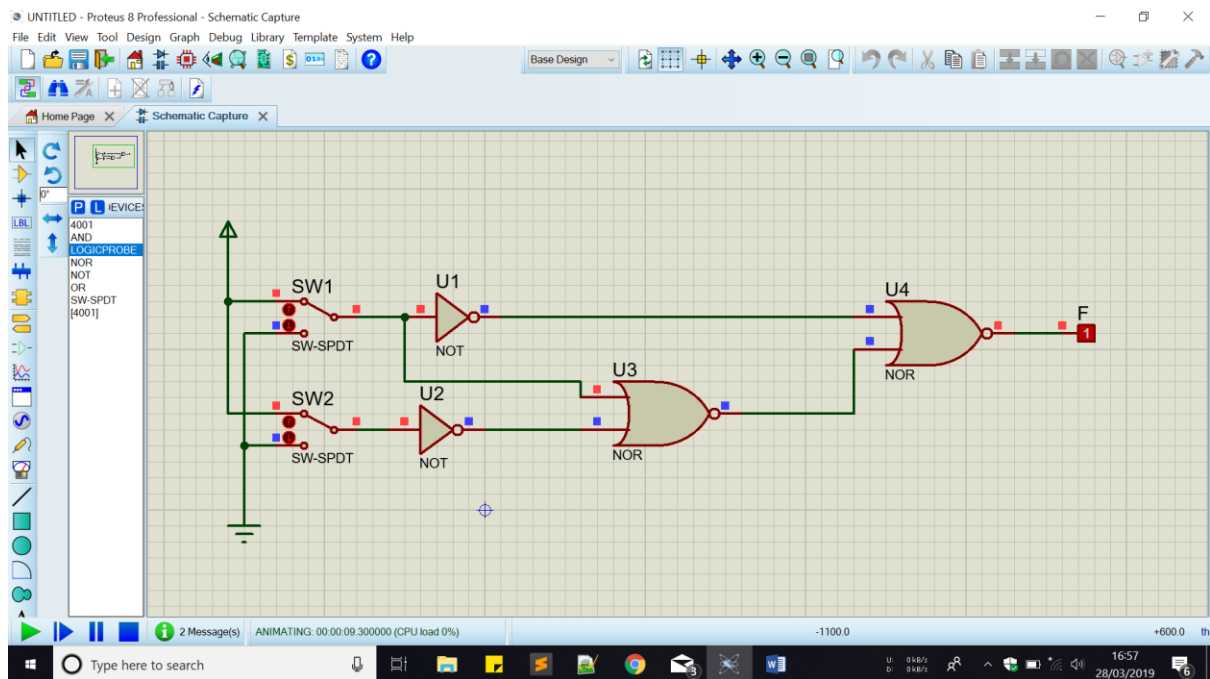

$$\begin{aligned}
 F &= \overline{\overline{X} + (X + Y)} \\
 &= \overline{\overline{X} + (X + Y)} \\
 &= X + (X + Y) \\
 &= X + Y
 \end{aligned}$$


a. Truth Table

X	Y	F
0	0	0
0	1	0
1	0	1
1	1	1

b. Time Diagram

--	--	--	--

Additional Experiment 2

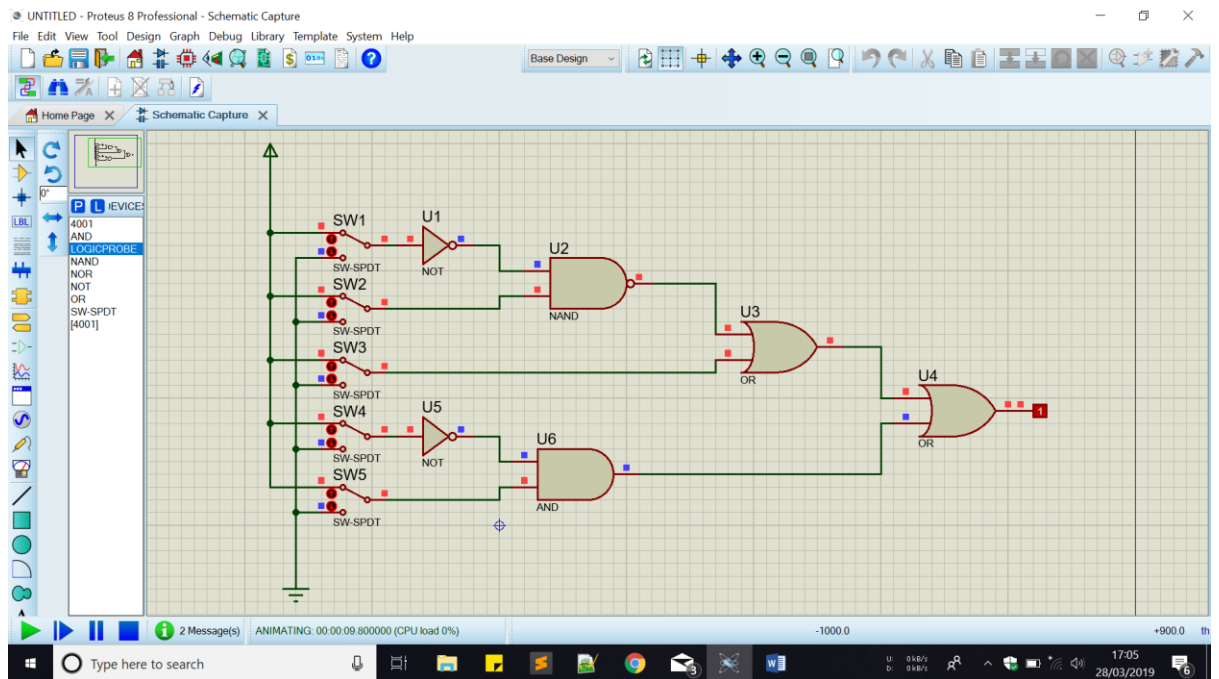

Picture 7.1 Set Get for Boolean Product Function $F = (\overline{A}B + C) + (\overline{D}E)$