

**PRACTICUM DIGITAL SYSTEM**

**MODUL 5**

**DIGITAL SYSTEM**



**By :**

**Donny Rizal Adhi Pratama**


**L200183161**

**INFORMATION TECHNOLOGY**

**FACULTY OF COMMUNICATION AND INFORMATICS**

**MUHAMMADIYAH UNIVERSITY OF SURAKARTA**

# Experiment 1

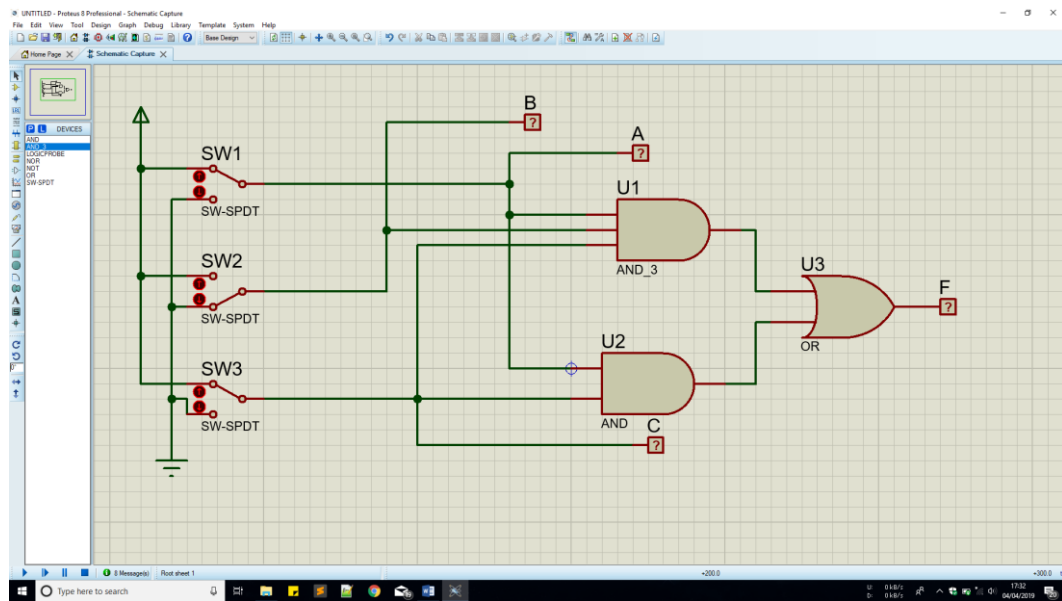

Picture 1.1. Logic gate combination

## 1. Boolean functions

$$F = ABC + AC$$

## 2. Truth table

A	B	C	F
0	0	0	0
1	0	0	0
0	1	0	0
1	1	0	0
0	0	1	0
1	0	1	1
0	1	1	0
1	1	1	1


## 3. Karnaugh map

		AB			
		00	01	11	10
C	0	0	0	0	0
	1	0	0	1	1

## 4. Boolean functions based on karnaugh map


$$F = AC$$

## 5. Logic gate combination based on new boolean functions

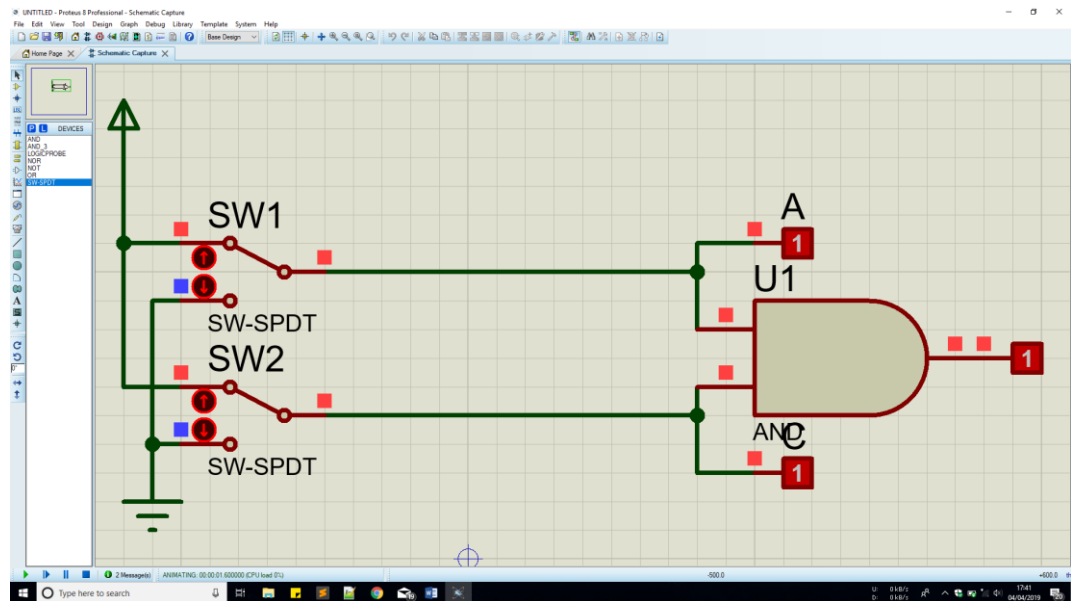

Picture 1.2. New logic gate combination

## Experiment 2

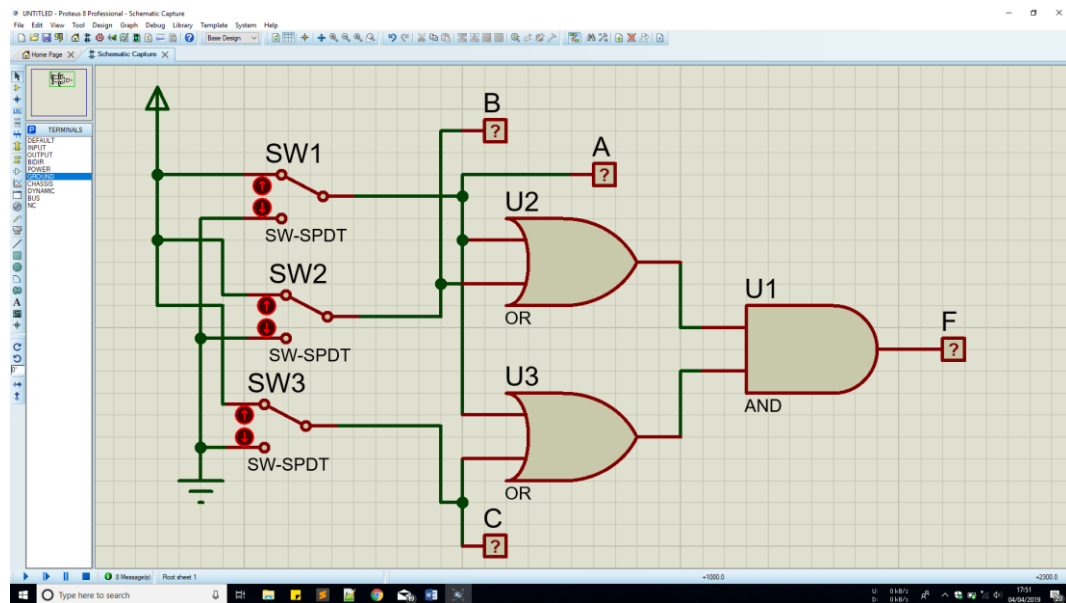

Picture 2.1. Logic gate combination

### 1. Boolean functions

$$F = ABC + AC$$

### 2. Truth table

A	B	C	F
0	0	0	0
1	0	0	1
0	1	0	0
1	1	0	1
0	0	1	0
1	0	1	1
0	1	1	1
1	1	1	1


### 3. Karnaugh map

		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	1

### 4. Boolean functions based on karnaugh map

$$F = A + BC$$


## 5. Logic gate combination based on new boolean functions

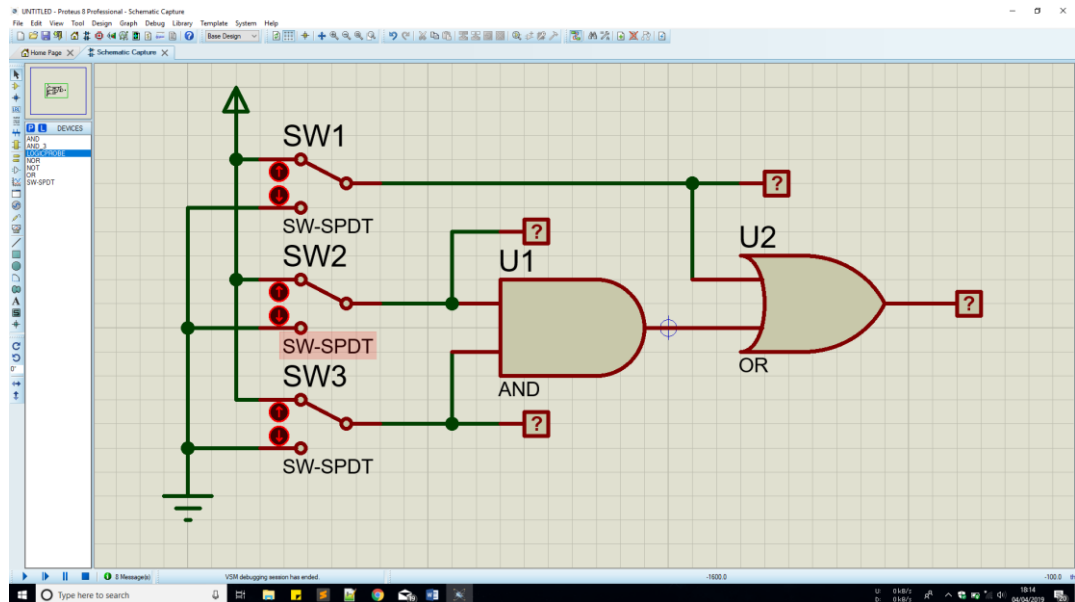

Picture 2.2. New logic gate combination

## Experiment 3

Picture 3.1. Logic gate combination

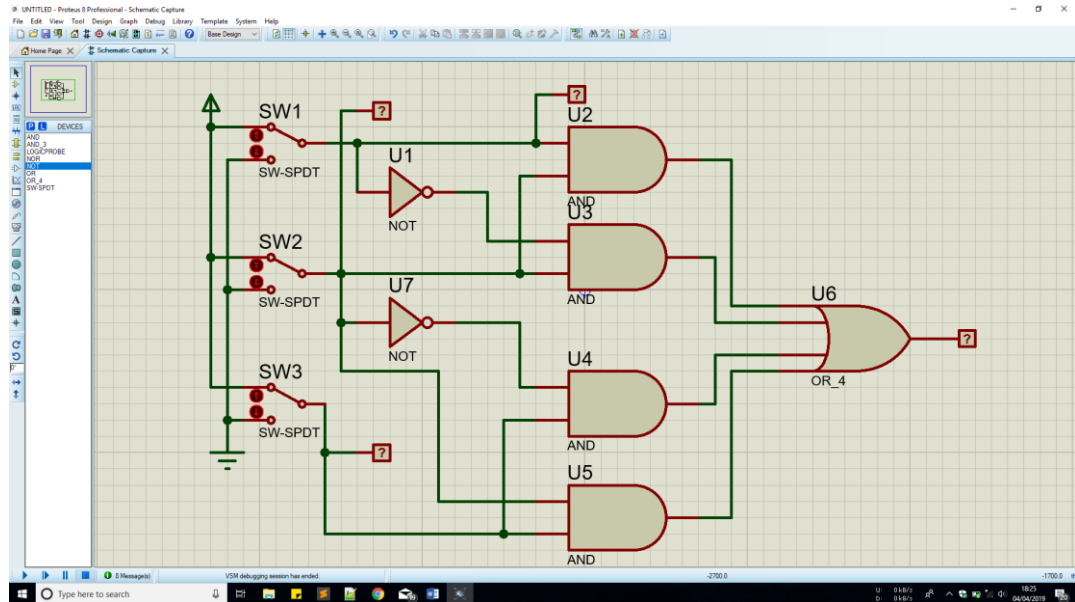

1. Boolean function

$$F = AB + A'B + B'C + BC$$

2. Truth table

A	B	C	F
0	0	0	0
1	0	0	0
0	1	0	1
1	1	0	1
0	0	1	1
1	0	1	1
0	1	1	1
1	1	1	1


3. Karnaugh map

		AB			
		00	01	11	10
C	0	0	1	1	0
	1	1	1	1	1

4. Boolean functions based on karnaugh map

$$F = B + C$$

## 5. Logic gate combination based on new boolean functions

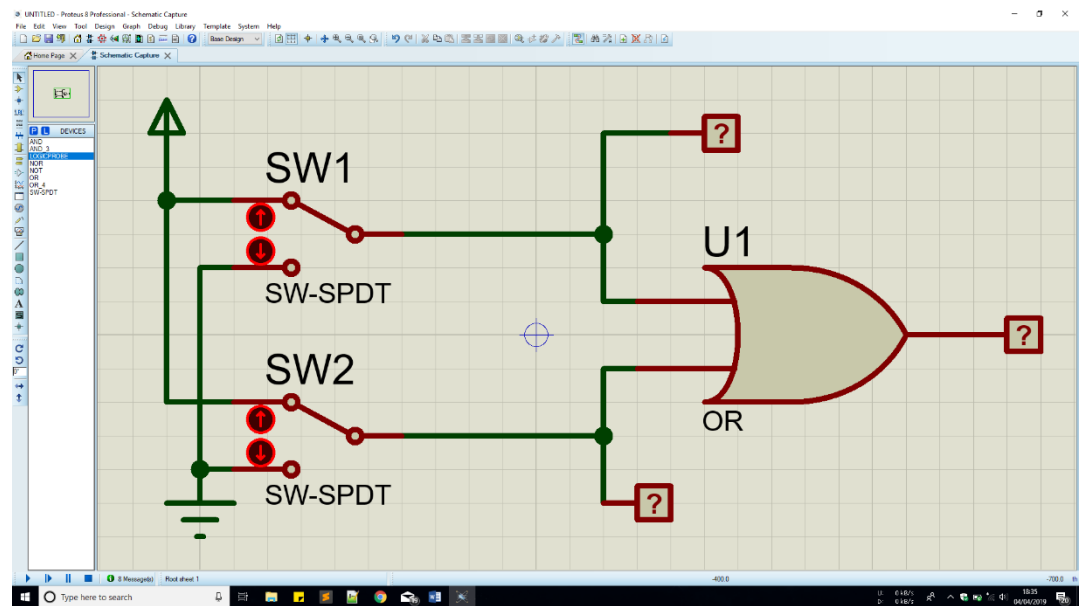

Picture 3.2. New logic gate combination